

Lab3: Push Button and LED Control



National Chiao Tung University
Chun-Jen Tsai
9/29/2017


Lab 2: Push Buttons and LED Control

- ❑ In this lab, you will use the FPGA development board “Arty” to implement a simple I/O control circuit
 - There are 4 push-buttons and 4 yellow LED lights on the board
 - You must design a synchronous circuit that reads each of the push-button inputs and display different light patterns on the board


- ❑ The deadline is on 10/10, 5:00 pm

Buttons and LEDs on the Arty Board

- ❑ The Arty FPGA development board:

 

 - ❑ We also have designed an I/O daughter board for Arty:




The System Behavior of Lab3

- ❑ Your circuit should have a 4-bit counter register
 - The counter value is set to zero upon reset
 - The counter value is a signed value in 2's complement format
 - The 4 LEDs display the 4 counter bits at all time
- ❑ Push-buttons #0 and #1 are used to decrease/increase the counter value:
 - Push the BTN1/BTN0 increases/decreases the counter by 1
 - If the counter value becomes greater than 7, it is truncated to 7; if the value is smaller than -8, it is set to -8
- ❑ Push-buttons #2 and #3 are used to control the brightness of the LEDs
 - BTN3 makes the LED brighter and BTN2 makes it darker

User I/O Pins of an FPGA IC

 - ❑ There are many “FPGA” pins that are used as user I/O pins: each pin connects to an I/O device such as the push-buttons or the LEDs:




Bottom-view of an FPGA IC
(shows IC pins)

Top-view of an FPGA IC
(shows IC markings)

FPGA Pin Coordinates

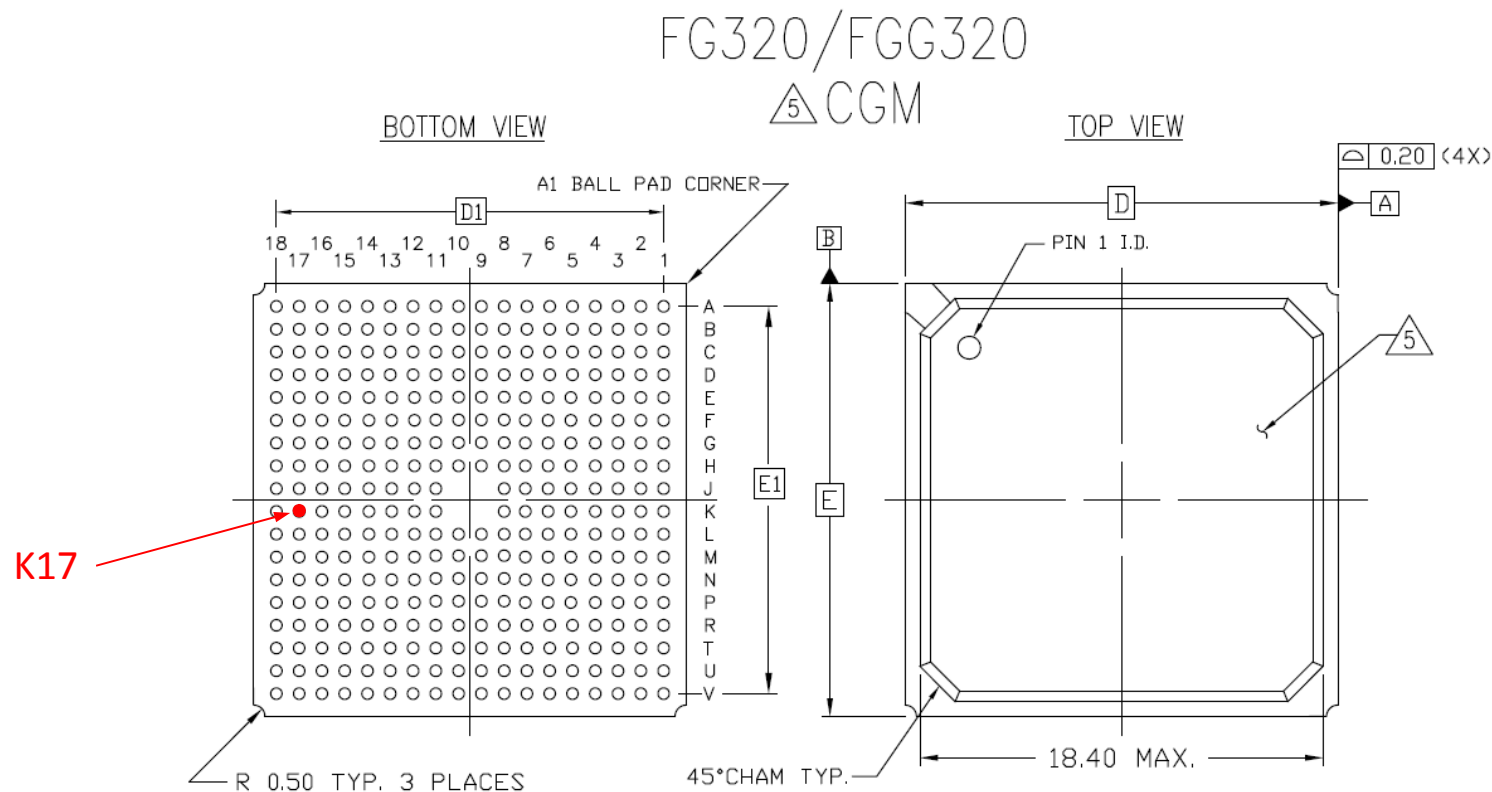- Each pin at the bottom of the FPGA has a coordinate. For example, “K17” is the coordinate of the red pin of the Xilinx FPGA IC in the “FG320” package:



Use the I/O Pin Signal in Verilog

- ❑ To read/write the I/O pins, we must map the pin coordinates to Verilog signals in our code
 - A user constraint file, *.xdc, is used to do the job
- ❑ A user constraint is a text command that specifies the physical property in an HDL code. For example, for the four push-buttons, their mapping to Verilog signals can be as follows:

```
set_property -dict { PACKAGE_PIN D9 IOSTANDARD LVCMOS33 } [get_ports { usr_btn[0] }];  
set_property -dict { PACKAGE_PIN C9 IOSTANDARD LVCMOS33 } [get_ports { usr_btn[1] }];  
set_property -dict { PACKAGE_PIN B9 IOSTANDARD LVCMOS33 } [get_ports { usr_btn[2] }];  
set_property -dict { PACKAGE_PIN B8 IOSTANDARD LVCMOS33 } [get_ports { usr_btn[3] }];
```


IC pin coordinates

Signal type

Signal names to be used
in your Verilog code!

How to Read the Input Push-Button

 - ❑ The physical connection from an FPGA I/O pin to a push-button is as follows:




- ❑ Ideally, when a push-button is pushed (the circuit is closed), the FPGA pin that connects to the button becomes high voltage and the corresponding signal in Verilog reads “1”, otherwise it reads “0”.


The Bouncing Problem

- ❑ In reality, however, the signal value oscillates between 0 and 1 several times before it stabilizes. This is called the bouncing behavior of a hardware button.

The physical voltage values:

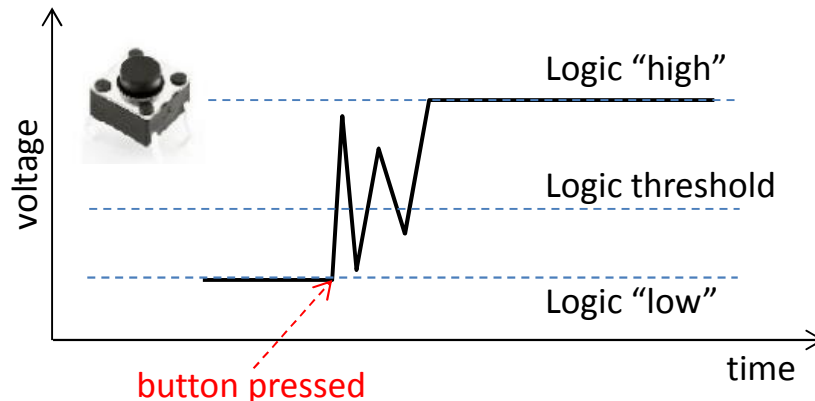

The actual digital signal:

 

The De-bouncing Circuit

- ❑ To detect whether the button has been pressed, you cannot simply check the button signals:

```
always @(posedge clk, posedge reset)
  if (reset == 1)
    BTN0_is_pressed = 0;
  else
    BTN0_is_pressed = (usr_btn[0]) ? 1 : 0;
```




- This circuit will catch all the state changes during the bouncing period → a single button click will be treated as multiple clicks!
- ❑ You must find a way to average-out the noises of the push-button signal during the bouncing period
 - Hint: you can use a shift register to accumulate the input signal; or a timer to wait out the bouncing period

Turn On/Off the LEDs

- ❑ The LEDs can be turned on/off by writing 1/0 to the corresponding Verilog signals, `reg [3:0] usr_led`
 - The LED constraint definitions:
 
```
set_property -dict { PACKAGE_PIN H5  IOSTANDARD LVCMOS33 } [get_ports { usr_led[0] }];  
set_property -dict { PACKAGE_PIN J5  IOSTANDARD LVCMOS33 } [get_ports { usr_led[1] }];  
set_property -dict { PACKAGE_PIN T9   IOSTANDARD LVCMOS33 } [get_ports { usr_led[2] }];  
set_property -dict { PACKAGE_PIN T10  IOSTANDARD LVCMOS33 } [get_ports { usr_led[3] }];
```



Clock and Reset Pins

- ❑ For synchronous design, you need a clock signal for your circuit
 - The clock signal usually comes from an on-board oscillator
 - There is an FPGA pin that connects to the oscillator

```
set_property -dict {PACKAGE_PIN E3 IOSTANDARD LVCMOS33} [get_ports { clk }];
```

- ❑ For the Arty board, the reset pin is the red push button defined as follows:

```
set_property -dict {PACKAGE_PIN C2 IOSTANDARD LVCMOS33} [get_ports { reset_n }];
```

Sample Project of Lab3

- ❑ A sample project, lab3.zip, is available on E3
 - The constraint file for Arty is provided to you in this project
- ❑ The project has a circuit that lights up LED 0 ~ 3 when you press BTN 0 ~ 3, respectively

```
module lab3(  
    input  clk,           // System clock at 100 MHz  
    input  reset_n,       // System negative reset signal  
    input  [3:0] usr_btn,  // Four user pushbuttons  
    output [3:0] usr_led   // Four yellow LEDs  
);  
  
assign usr_led = usr_btn;  
endmodule
```

- ❑ There is no de-bouncing circuit for the button inputs so you have to add this part by yourself

Generate the Programming File

- ❑ To test the design on Arty, you must generate the programming file “lab3.bit” for the FPGA:

The screenshot shows the Vivado 2017.2.1 IDE interface. The top menu bar includes File, Edit, Flow, Tools, Window, Layout, View, and Help. The top status bar shows 'write_bitstream Complete' with a green checkmark. The left sidebar contains the 'Flow Navigator' with sections for PROJECT MANAGER, IP INTEGRATOR, SIMULATION, RTL ANALYSIS, SYNTHESIS, and IMPLEMENTATION. The 'PROGRAM AND DEBUG' section is expanded, and the 'Generate Bitstream' button is highlighted with a red dashed circle and an arrow pointing to it. The 'PROJECT MANAGER - lab3' window shows the 'Sources' tab with 'Design Sources (1)' and 'Constraints (1)'. The 'Source File Property' window for 'arty_base.xdc' is open. The 'Project Summary' window shows the Verilog code for 'lab3.v'. The 'Design Runs' table at the bottom shows the synthesis and bitstream generation results.

Flow Navigator

- PROJECT MANAGER
 - Settings
 - Add Sources
 - Language Templates
 - IP Catalog
- IP INTEGRATOR
- SIMULATION
- RTL ANALYSIS
- SYNTHESIS
- IMPLEMENTATION
- PROGRAM AND DEBUG
 - Generate Bitstream
 - Open Hardware Manager

PROJECT MANAGER - lab3

Sources

- Design Sources (1)
- Constraints (1)
 - constrs_1 (1)
 - arty_base.xdc

Source File Property

arty_base.xdc

General Properties

Project Summary

lab3.v


```
22
23 module lab3(
24     input  clk,           // System clock at 100 MHz
25     input  reset_n,       // System reset signal, in negative logic
26     input  [3:0] usr_btn, // Four user pushbuttons
27     output [3:0] usr_led  // Four yellow LEDs
28 );
29
30 assign usr_led = usr_btn;
31
32 endmodule
33
```

Design Runs

Name	Constraints	Status	WNS	TNS	WHS	THS	TPWS	Total Power	Failed Routes	LUT	FF
synth_1	constrs_1	synth_design Complete!								0	0
impl_1	constrs_1	write_bitstream Complete!	NA	NA	NA	NA	NA	0.065	0	0	0


Downloading Your Circuit to the Board

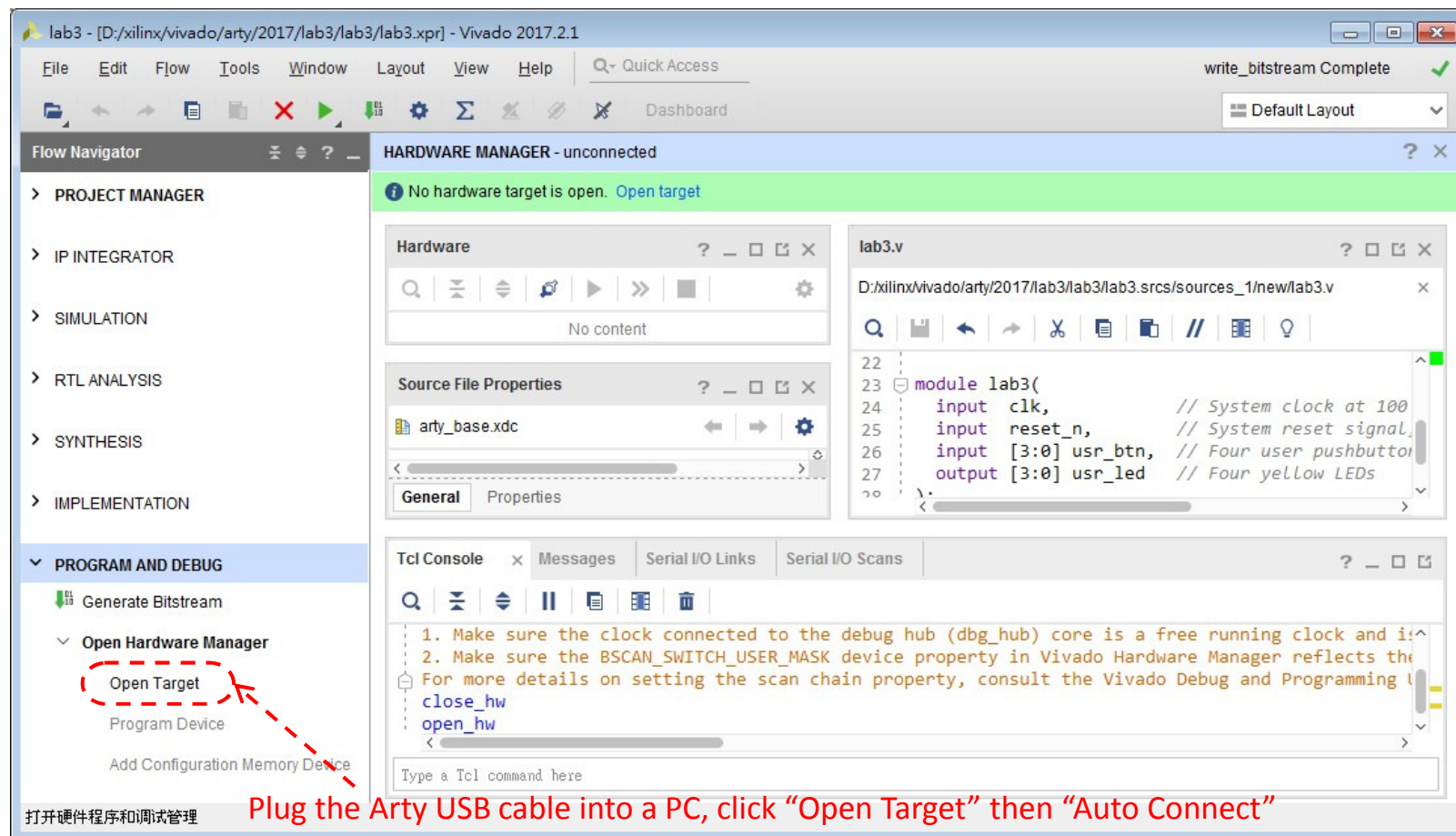- ❑ To download your programming file into the FPGA, you must use the “Hardware Manager” :




Program the FPGA

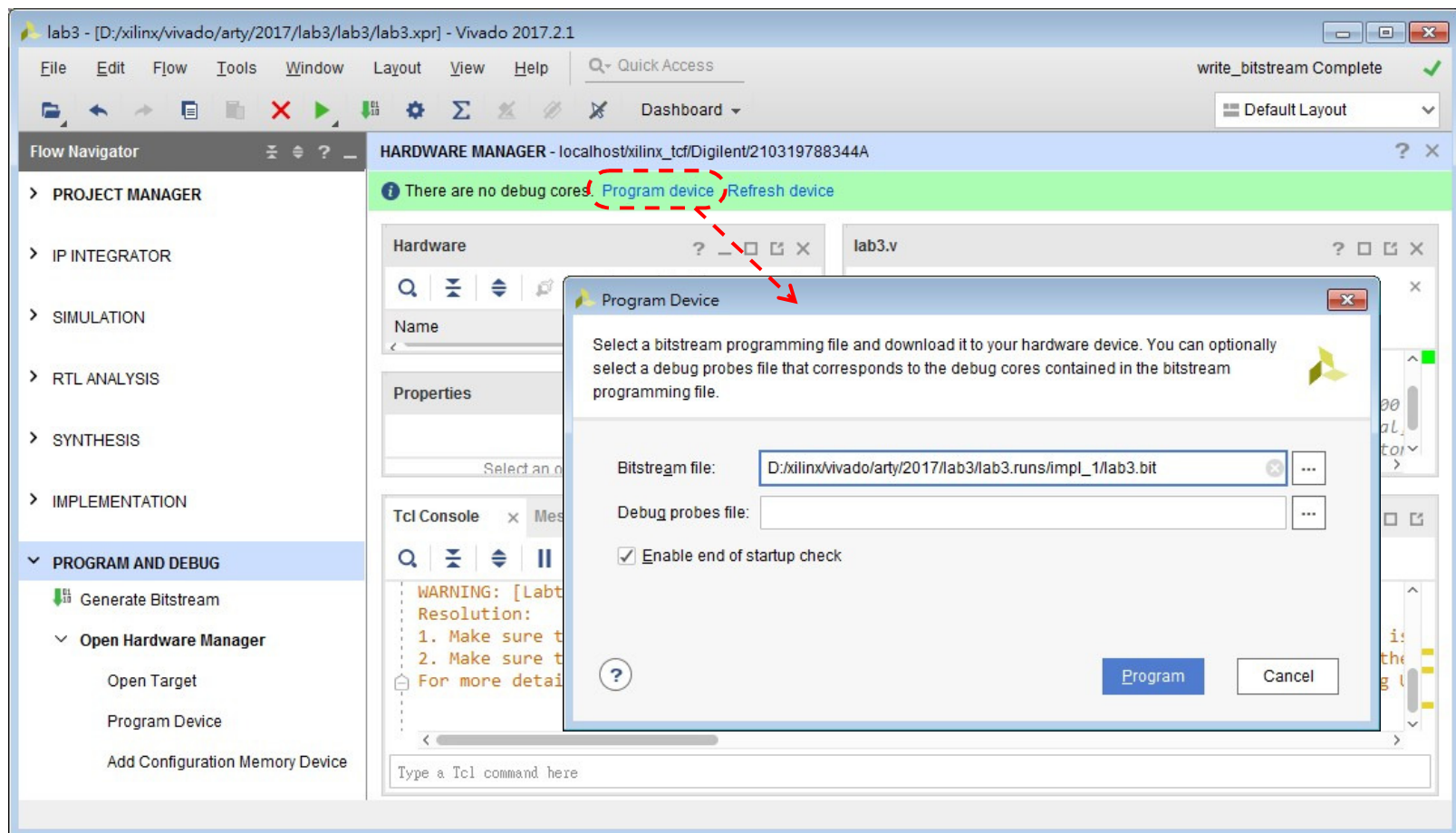- ❑ Hit “Program device” then browse to the *.bit file:
 - The bit file is under <project directory>/lab3.run/impl_1/lab3.bit




Test Your Design

 - ❑ You can now test your circuit by clicking the buttons on the Arty board and see how the LEDs lights up!



What You Need to Do for Lab 3

 - ❑ Design a circuit to display the value of a 4-bit signed counter on the LEDs with different brightness
 - BTN1/BTN0 increases/decreases the counter value
 - BTN2/BTN1 increases/decreases the brightness of the LEDs (all LEDs have the same brightness simultaneously)



Increase/decrease the brightness of LEDs with five different brightness levels


Increase/decrease the 4-bit counter value between $-8 \sim 7$

Control of the LED Brightness

- ❑ The LED device in the Arty board can only be fully lit (full power) or turned off (zero power), you can not set it to different levels of brightness
- ❑ To trick your eyes to see different levels of brightness, you can send a PWM signal to its power input
- ❑ A PWM input to the LED turns it on-an-off quickly
 - The persistence of human visions will not see flickering but only different levels of brightness, as long as your PWM frequency is high enough

A PWM Signal

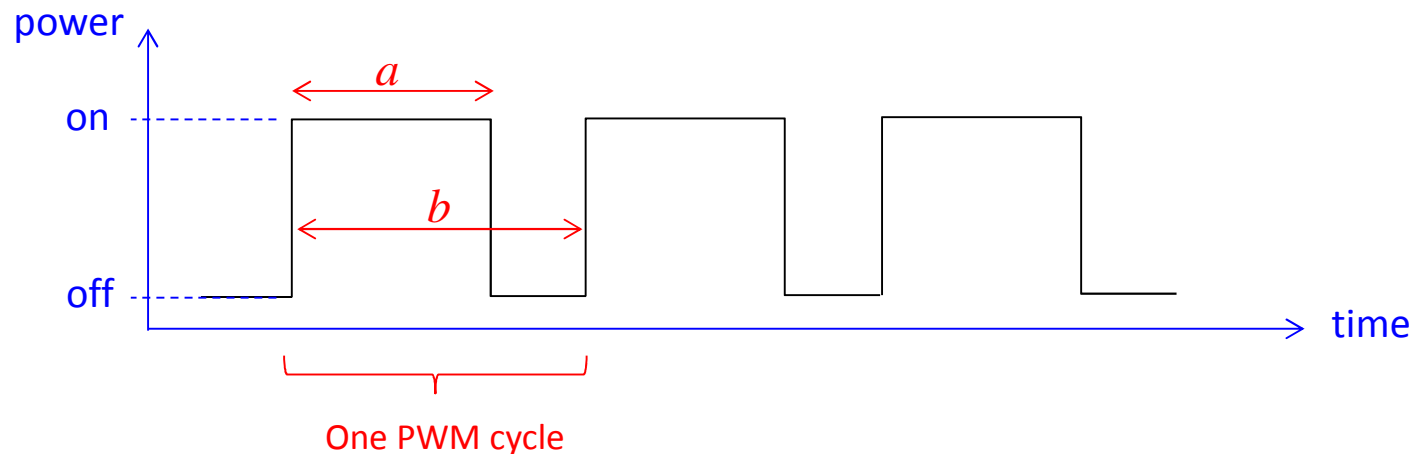
- ❑ A PWM signal is simply a square wave signal:



- ❑ Duty-cycle: the percentage of one cycle of PWM that is in “on” state (i.e., $(a/b) \times 100\%$ in the figure)
 - 50% duty-cycle means the signal is “on” half of the time


Generation of a PWM Signal

 - ❑ The system clock of our boards is 100MHz
 - Each second has 100,000,000 clock ticks
- ❑ To generate a 100 Hz PWM signal, the full cycle period would be equal to 1,000,000 clock ticks
 - The clock ticks for a 25% duty cycle PWM signal @ 50Hz would be 250,000 clock ticks for “on” period and 750,000 clock ticks for “off” period



PWM Control of Brightness

 - ❑ Persistence of visions make most people do not see flickering when the LED is switching faster than 60 Hz
- ❑ We can use a PWM signal higher than 60Hz to control the brightness of an LED
- ❑ The PWM duty cycle determines the brightness



Brightness Control for Lab3

- ❑ In Lab3, you must design a PWM signal generator circuit
 - The PWM signal must have a frequency of 100 Hz and five different duty cycles: 5%, 25%, 50%, 75%, and 100%
 - If an LED should be turned on, the PWM signal will be assigned to `usr_led[]`
 - If an LED should be turned off, 0 will be assigned to `usr_led[]`
 - BTN3 increases the current duty cycle, and BTN2 decreases the current duty cycle