

# Lab 10: VGA Graphic Display



National Chiao Tung University  
Chun-Jen Tsai  
12/19/2017

# Lab 10: VGA Graphic Display

---

- ❑ In this lab, you will implement a circuit that shows some graphics using the VGA video interface; your circuit must do the following things:
  - Animates the moon to move across the picture with green-screen removal
  - Adds fireworks animations to the picture



- ❑ The deadline of the lab is on 1/2


# Lab 10 Setup

- ❑ In lab 10, the Arty board will share the LCD monitor with the PC
  - To see the video output of Arty, you must press the “video source” toggle on the LCD monitor to change the video source from “DVI” (for PC) to “VGA” (for Arty)
  - You should press “MENU” → “Image” → “Aspect Control” and set it to 4:3.



 
# VGA – Old Soldiers Never Die

- ❑ VGA stands for Video Graphics Array; it's a video interface originally designed for CRT display


 
# VGA Scanning Pattern


- ❑ A VGA screen displays the entire screen pixel-by-pixel:
  - The pixels of the screen are illuminated following a one-dimensional scanning path
  - When pixel at  $(x, y)$  are “scanned,” your circuit must tell the screen what RGB color it should display



# VGA Interface Pin Assignment
 
## ❑ VGA uses HD15 (a.k.a. D-sub) connectors

- Pin #1 Red (0 ~ 0.7V)
- Pin #2 Green (0 ~ 0.7V)
- Pin #3 Blue (0 ~ 0.7V)
- Pin #5, 6, 7, 8 Ground
- Pin #9 Power (for external I<sup>2</sup>C device)
- Pin #10 Sync Return (Sync Ground)
- Pin #4, 11 No connection
- Pin #12 I<sup>2</sup>C SDA
- Pin #15 I<sup>2</sup>C SCL
- Pin #13 Horizontal Sync (2.5V)
- Pin #14 Vertical Sync (2.5V)




HD-15 male

# VGA Signal Timing (1/2)
 
## □ Horizontal Retrace Cycles (for 640×480@60Hz):


- $1/31.77\mu\text{s} = 31476 \text{ Hz}$
- $31476/60 = 525 \text{ lines/frame}$



Parameters	A	B	C	D	E
Time	31.77μs	3.813μs	1.907μs	25.42μs	0.6356μs
 
# VGA Signal Timing (2/2)

- ❑ Vertical Retrace Cycles (for 640x480@60Hz):
  - $1/16.66\text{ms} = 60\text{ Hz}$  (frames/second)




Parameters	O	P	Q	R	S
Time	16.68ms	63.56μs	1.049ms	15.25ms	0.3178ms


 
# Sync Timing in Pixel Clocks


- ❑ The Horizontal Sync (HS) and Vertical Sync (VS) signal in pixel clock ticks are as follows:



Format	Sync Type	Clock	Total	$T_{RGB}$	$T_{FP}$	$T_{SW}$	$T_{BP}$
VGA (4:3 Screen) 640x480@60Hz	HS (pixels)	25.175MHz	800	640	48	96	16
	VS (lines)		525	480	10	2	33
VGA (4:3 Screen) 800x600@72Hz	HS (pixels)	50 MHz	1040	800	56	120	64
	VS (lines)		666	600	37	6	23

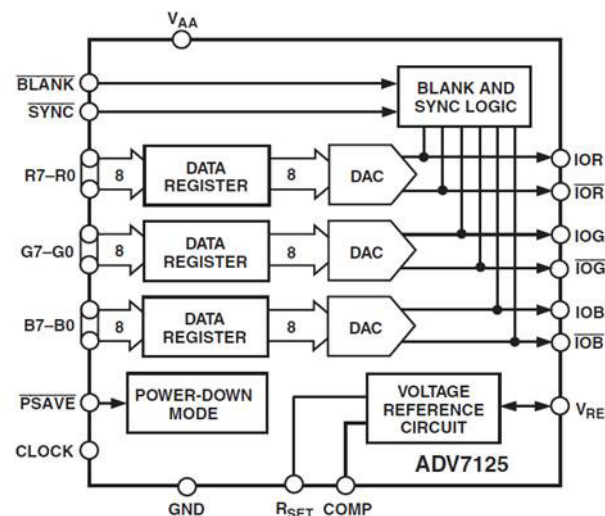
# Digital-to-Analog Conversion

- ❑ VGA is an analog interface
  - 0v stands for the darkest pixel, 0.7v stands for the brightest
  - The transition from darkest pixel to brightest pixel is not linear
- ❑ A video digital-to-analog converter (DAC) IC is usually used to convert digital pictures to analog VGA signals
  - The most popular DAC is the ADV 7125 IC by Analog Devices



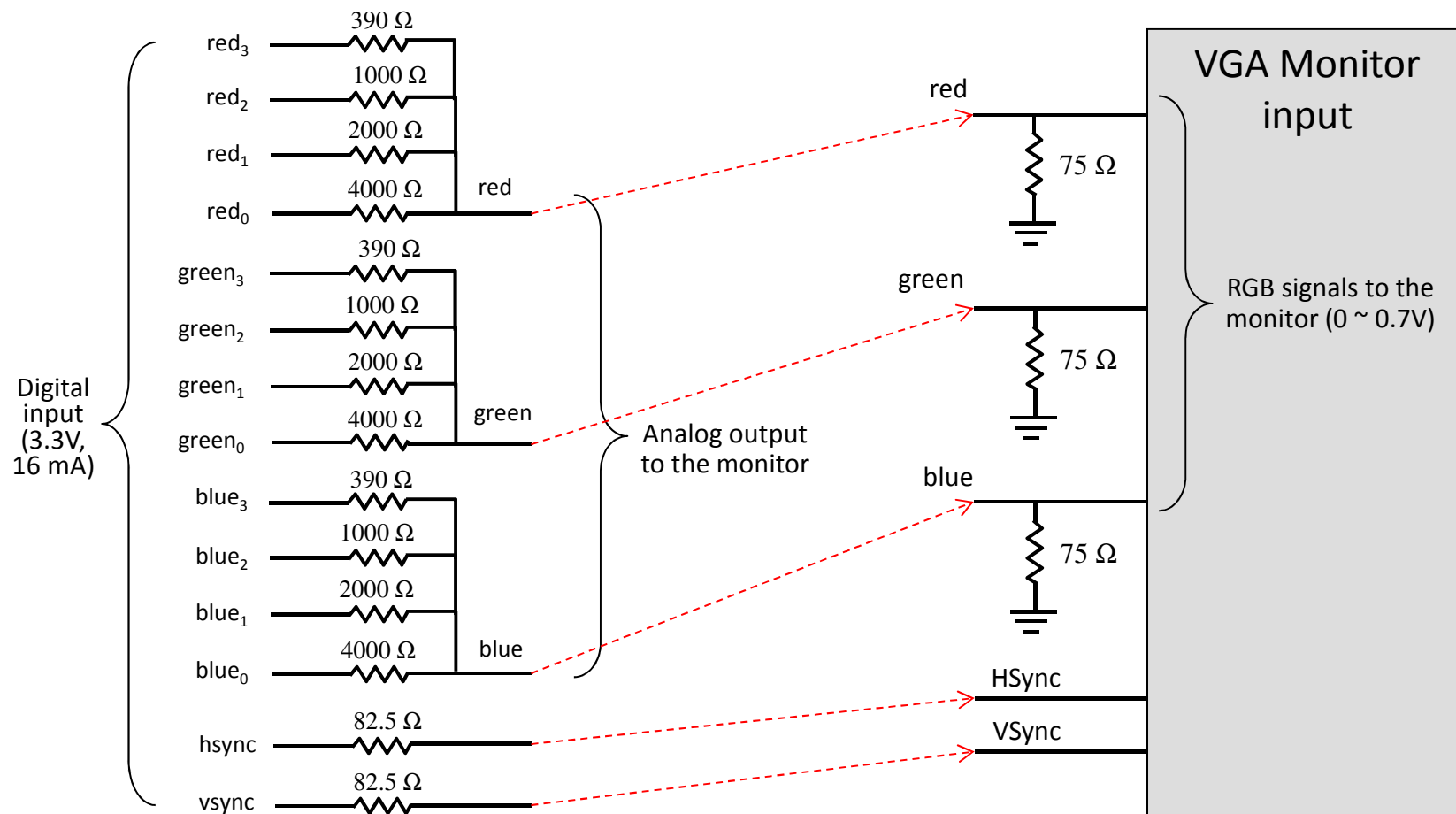
# Simple VGA Interface Circuit

- ❑ A resistor network is used on the I/O board of Arty to provide a 3×4-bit VGA DAC:


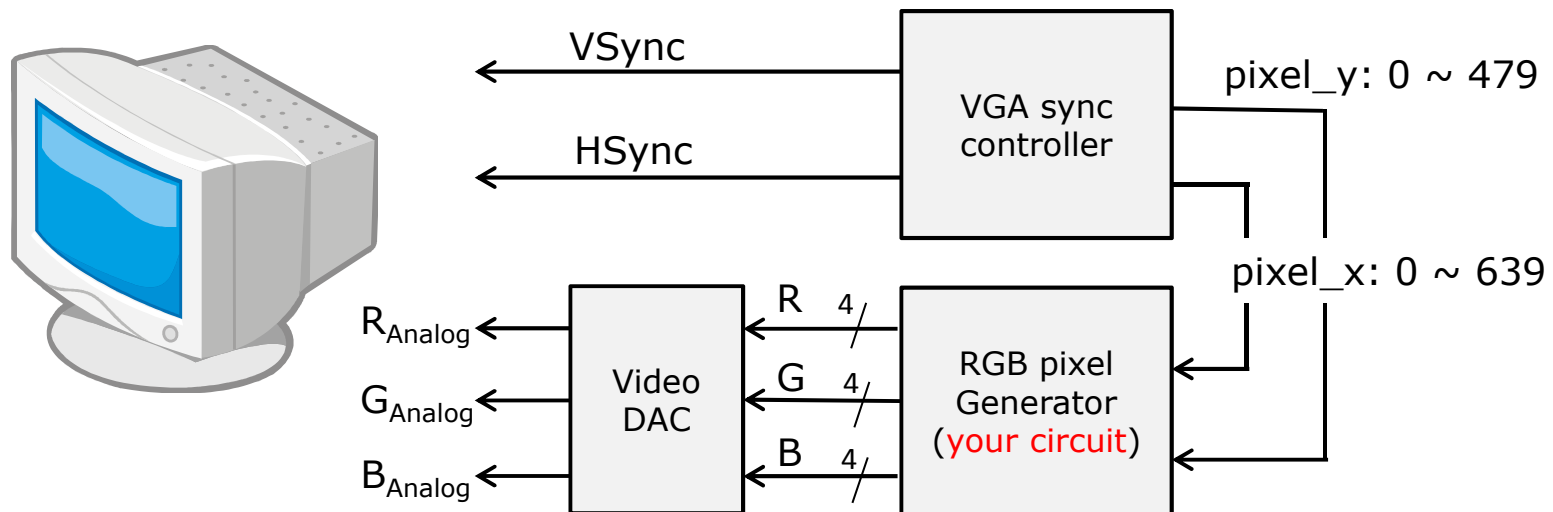
# VGA Controller for Lab 10

- ❑ The Verilog code of a VGA synchronization controller will be provided for this lab:



# VGA Sync Controller Interfaces

- ❑ The I/O port of the VGA controller module:

```
module vga_sync
(
    input clk,
    input reset,
    output wire oHS,
    output wire oVS,
    output wire visible,
    output wire p_tick,
    output wire [9:0] pixel_x,
    output wire [9:0] pixel_y
);
```


Is it active scan line  
period or sync period?

Ready to get next pixel?

\* When “visible” is false, the RGB output to the monitor MUST be all zeros!

 
# Computer Graphics and Video Buffer

- ❑ Processors are too slow to directly generate pixel data for video display
  - Old arcade games are built using dedicated circuit to produce graphics
- ❑ A break-through idea that enables software-based computer graphics is the concept of frame buffers (FB):


 
# Double-Frame Buffering

- ❑ Computer systems usually use a single-port memory for video frame buffer
  - Most memory bandwidth will be used by the video controller
  - CPU cannot make significant update to the content of the frame buffer without interrupting the video controller
- ❑ Double frame buffers can be used to solve this problem



# Cycle Stealing from the Retrace Time

---

- ❑ Some systems do not have enough memory for double-buffering, other tricks must be used to modify the FB without interfering the video controller
- ❑ During the horizontal or vertical retrace periods, the video controller is NOT reading the FB
- ❑ FB data modifications during the sync periods will not corrupt video



 
# Good News for Lab 10

- ❑ In lab 10, you do not have to modify the video FB
  - The video FB is only used to store the background image
  - All foreground objects are generated by your circuit on-the-fly
- ❑ For example, the moving moon in the sky is done by:



A 320x240-pixel background image stored in the 12-bit SRAM.




A 64x40-pixel foreground image stored in the same SRAM. The green pixels are transparent pixels that shall not be displayed.



You must replace the green pixels by the background pixels.

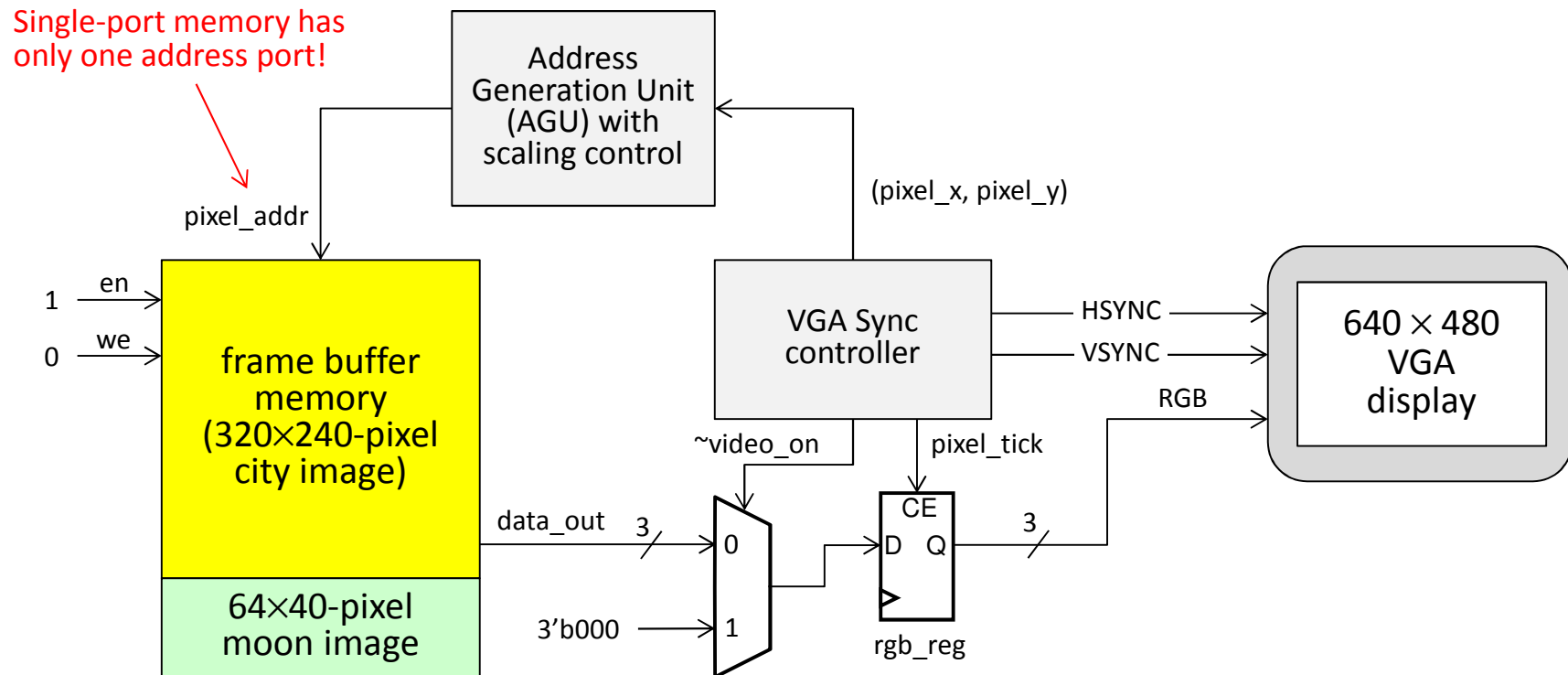
# Sending Frame Buffer Content to VGA

- ❑ The frame buffer in the SRAM can be connected to the VGA controller as follows:


 
# Image Scaling

- ❑ The size of our frame buffer has  $320 \times 240$  pixels, but the VGA resolution is of  $640 \times 480$  pixels → we must blow up the picture by  $2 \times$  in each dimension
- ❑ A simple scaling algorithm can be used:
  - Each pixel in the frame buffer is used repeatedly for four pixels on the screen



# Sample Code of the AGU with Scalar

- ❑ The address generation unit and the RGB register can be coded as follows:

You can change this to a combinational block, but the critical path will be longer

```
// ----- AGU -----
always @ (posedge clk) begin
    if (reset)
        pixel_addr <= 0;
    else
        // Scale up a 320x240 image for the 640x480 display.
        // (pixel_x, pixel_y) ranges from (0,0) to (639, 479)
        pixel_addr <= (pixel_y >> 1) * VBUF_W + (pixel_x >> 1);
end

// ----- RGB register -----
always @(posedge clk) begin
    if (pixel_tick) rgb_reg <= rgb_next;
end

always @(*) begin
    if (~video_on)
        rgb_next = 3'b000; // Sync period, must set rgb to zeros
    else
        rgb_next = data_out; // RGB value at (pixel_x, pixel_y)
end
```


# Video Frame Buffer for Lab 10

---

- ❑ In lab 10, we declare a 12-bit SRAM with  $320 \times 240 + 64 \times 40$  cells to store the city image and the moon image
  - The first  $320 \times 240$  cells are also used as the video frame buffer
  - Address 0 is the start address of the video buffer (i.e., the city image)
  - Address  $320 \times 240$  is the start address of the moon image
- ❑ The SRAM has only one port → the circuit cannot read from the video frame buffer and read the moon image at the same clock cycle!
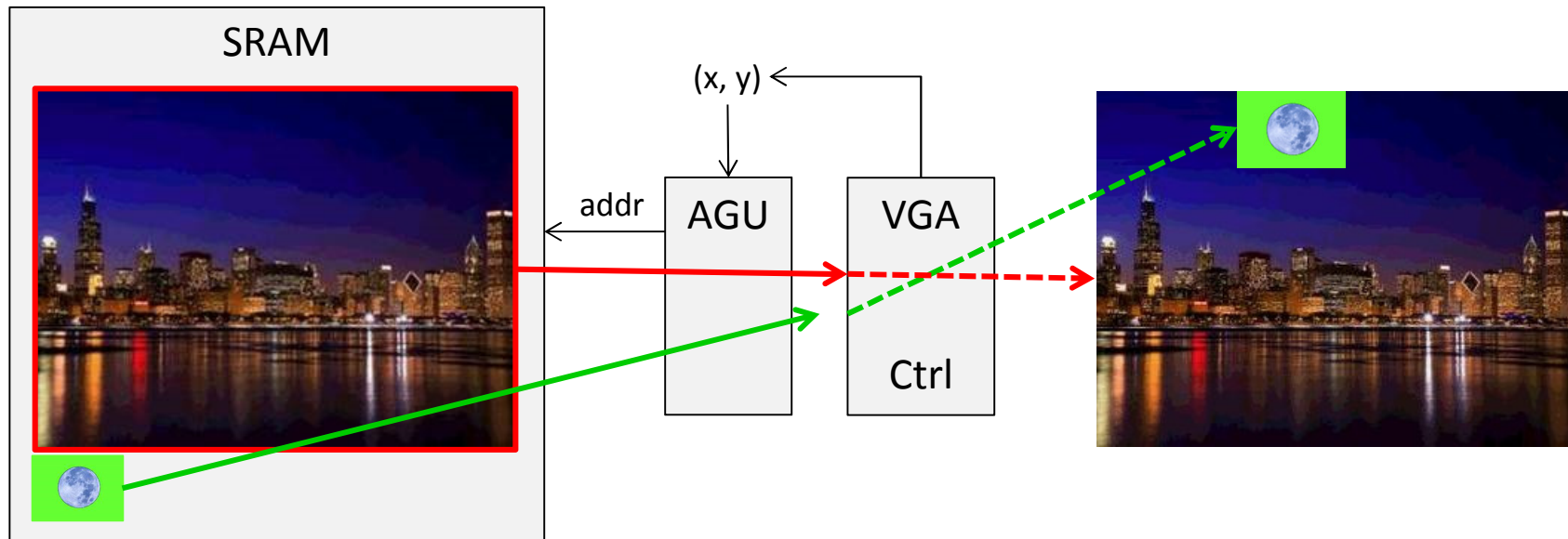
# The Sample Code in Lab 10

- ❑ A simple way to overlay the moon image on the city image is to read from the moon image if  $(x, y)$  falls in the moon area; otherwise, read from the city image:




# Green Screen Technique

- ❑ Green screens are often used in video production to overlay foreground objects on a background shot at a different location
  - Green pixels of the foreground images will be replaced by the background image pixels at the same coordinates


 
# What You Need to Do for Lab10?

- ❑ First, you must replace the green pixels of the moon image by the co-located background pixels (60 points)
- ❑ Secondly, you must use your imaginations to create some fireworks animations in the sky area (40 points)



Lab 10 sample code



Green-screen blending



Pretty fireworks

Your tasks for lab 10!